

## ASDV 1205, Digital Design Lab

1. Design the circuit: Assume a room has three doors and a switch by each door controls a single light in the room.

- Let A, B, and C denote the state of the switches
- Assume the light is off if all switches are off
- Turning on any switch turns the light on. Turning off another switch will have to turn the light off.
- Light is on if any one switch is on and off if two (or no) switches are on.
- Light is on if all three switches are on

A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

2. Car safety alarm

- Design a car safety alarm considering four inputs

- Door closed (D)

-Key in (K)


- Seat pressure (S)

- Seat belt closed (B)

- The alarm (A) should sound if

- The key is in and the door is not closed, or

- The door is closed and the key is in and the driver is in the seat and the seat belt is not closed




### Car safety alarm

D	K	S	B	A
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

$$A(D,K,S,B) = \sum m(4,5,6,7,14)$$
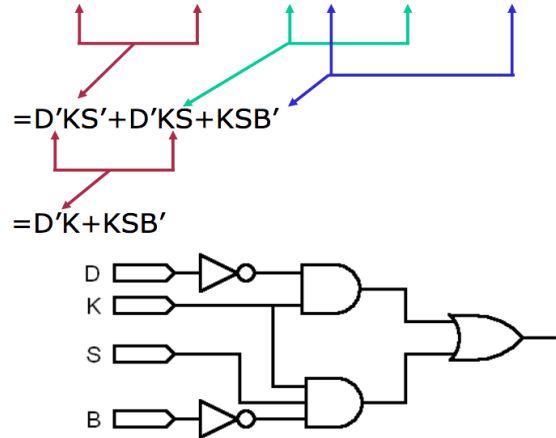
$$A(D,K,S,B) = D'KS'B' + D'KS'B + D'KSB' + D'KSB + DKSB'$$



Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 5-9