
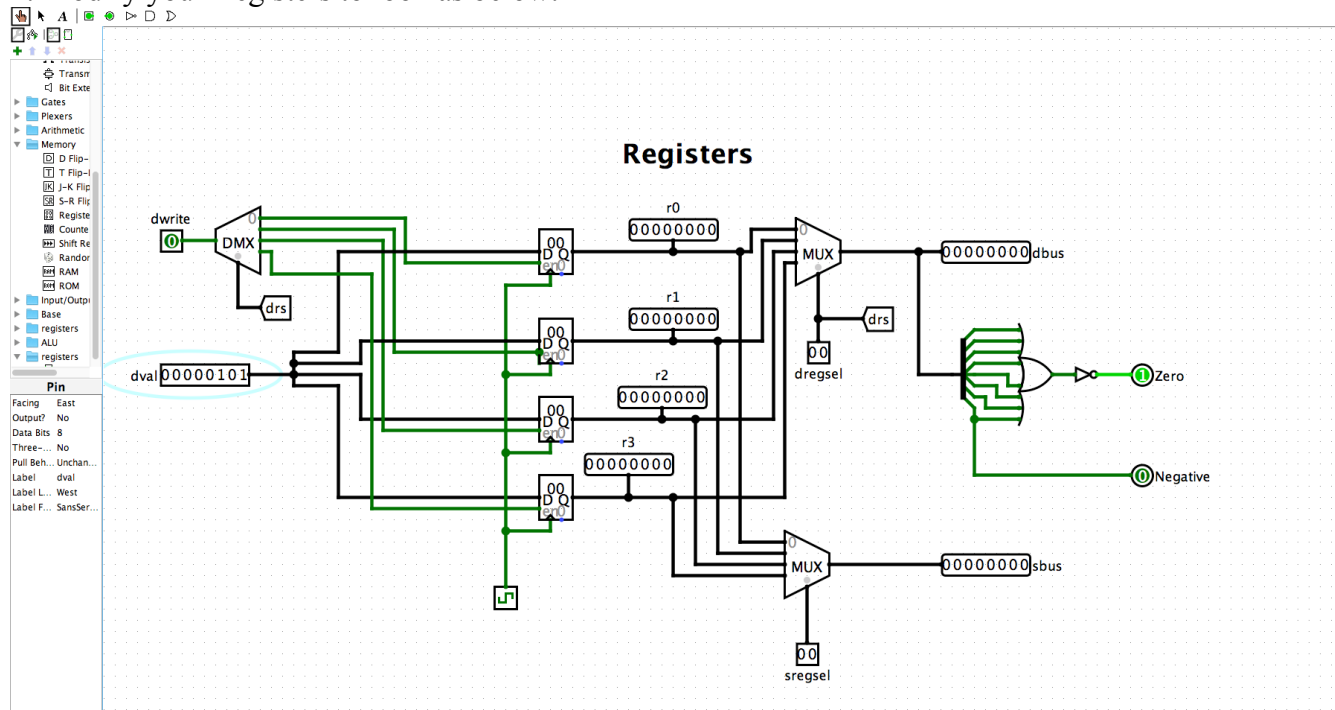


ASDV 1205 Lab

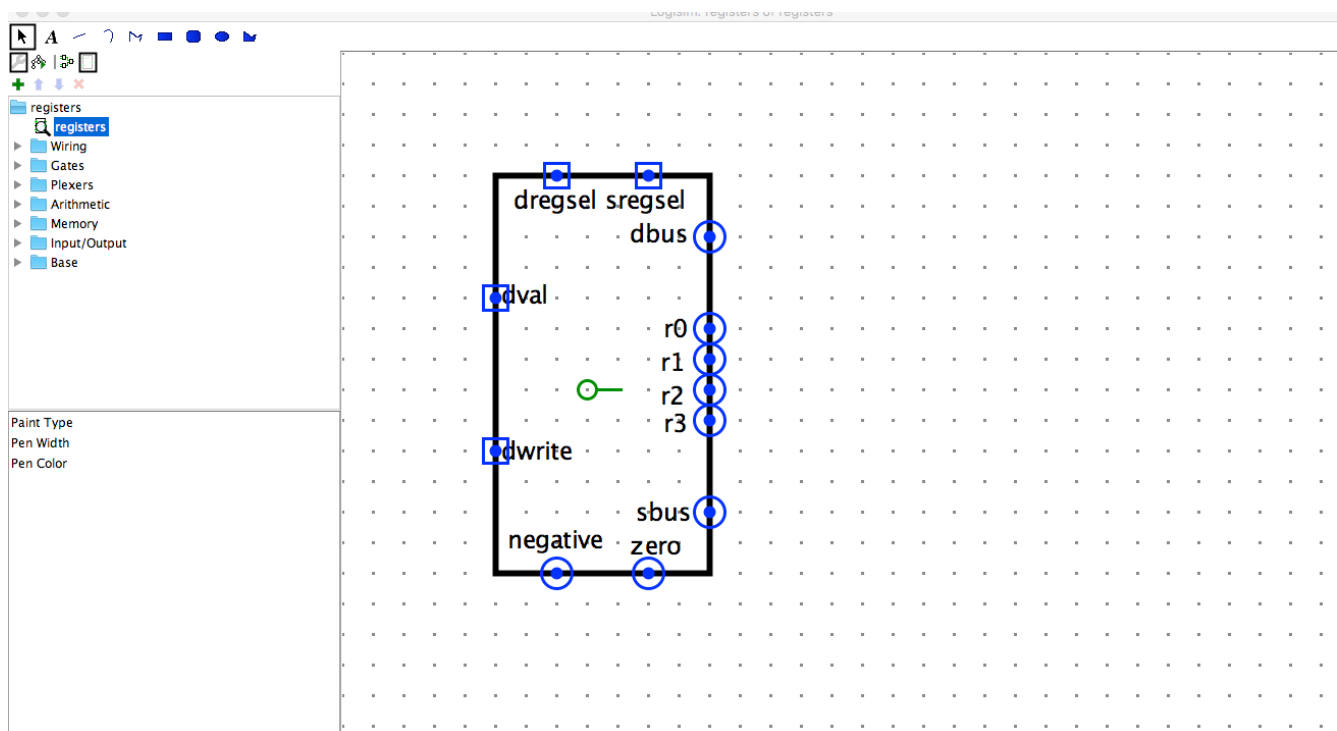1. Modify your Registers to look as below:



2. Design the Register chip.



3. Create new File, load ALU, Registers and put in a RAM.
4. Test it by adding 1 + 4 to produce 5.

